

# VLSI Course Project

## 4-Bit CLA Adder

Snehil Sanjog

2023102051

snehil.sanjog@students.iiit.ac.in

### INTRODUCTION

4 Bit Carry Look Ahead (CLA) Adder adds two 4 bit numbers and gives the final 4 bit sum along with the 5th bit carry. However unlike normal 4 bit Ripple Carry Adder which calculates each carry one at a time, CLA Adder calculates all the carry at the same time hence reducing the propagation delay.

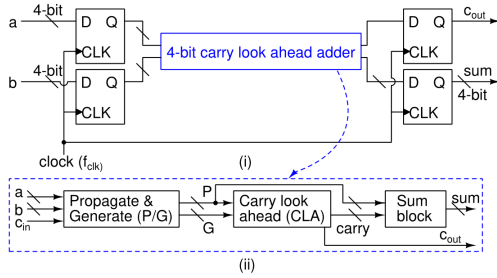


Fig. 1: Various circuit blocks for our Adder

### I. BASIC STRUCTURE FOR THE CLA ADDER

In Fig. 1 part (ii), we need to create the three blocks. First we generate the  $p_i$  and  $g_i$  (Propagate and Generate) for CLA block.

$$p_i = a_i \oplus b_i$$

$$g_i = a_i \cdot b_i$$

Then we calculate all carries in CLA block by following logic,

$$c_{i+1} = p_i \cdot c_i + g_i$$

From this, we can calculate all carries  $c_i$ 's from the propagates and generates ( $p_i$ 's and  $g_i$ 's).

$$c_1 = (p_0 \cdot c_0) + g_0$$

$$c_2 = (p_1 \cdot p_0 \cdot c_0) + (p_1 \cdot g_0) + g_1$$

$$c_3 = (p_2 \cdot p_1 \cdot p_0 \cdot c_0) + (p_2 \cdot p_1 \cdot g_0) + (p_2 \cdot g_1) + g_2$$

$$c_4 = (p_3 \cdot p_2 \cdot p_1 \cdot p_0 \cdot c_0) + (p_3 \cdot p_2 \cdot p_1 \cdot g_0) + (p_3 \cdot p_2 \cdot g_1) + (p_3 \cdot g_2) + g_3$$

Finally we can get the final sum by following logic,

$$S_i = p_i \oplus c_i$$

From this we can get circuit diagram shown in Fig. 2. For multiple input AND & OR gates, we have used multiple gates instead of one gate with multiple inputs.

 


Fig. 2: Circuit for CLA Adder

### II. DESIGN TOPOLOGY AND SIZING

#### A. CLA Adder

For XOR, AND & OR gates, we use PTL(Pass Transistor Logic) Topology and CMOS Topology for Inverters. Their circuit diagram along with sizes are given in figures below.

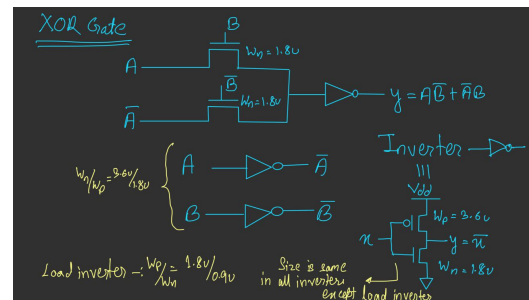


Fig. 3: Circuit for XOR gate and Inverter

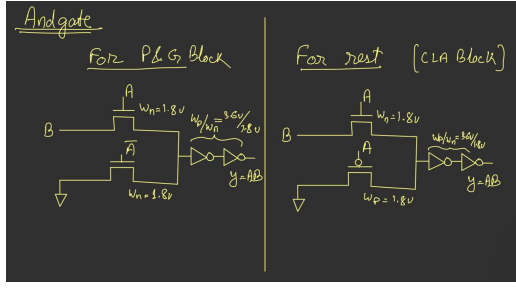


Fig. 4: Circuit for AND gate

 


Fig. 5: Circuit for OR gate

The Sizes are same for all the gates in CLA Adder.

### B. D-Flipflop

For D flipflop, we use TSPC (True Single Phase Clock) topology. Given below is the circuit for flipflop along with its size.

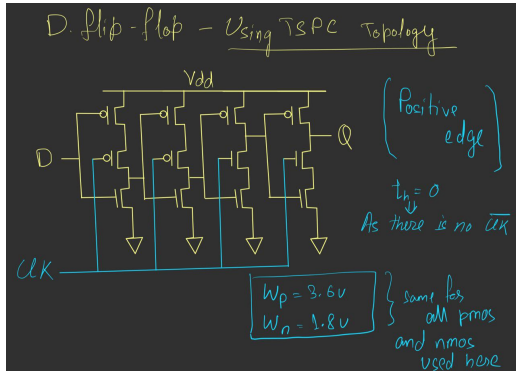


Fig. 6: Circuit for D FlipFlop with its sizes

## III. PRE-LAYOUT SIMULATIONS IN NGSPICE

### A. CLA Adder

For CLA Adder, we take input as  $a = 1001$  and  $b = 1101$  at  $t = 5ns$ . The output is as follows.

 


Fig. 7: Final Output for given inputs

The output is  $s = 10110$  which is correct for given input.

$$1001 + 1101 = 10110$$

Hence is working properly. As for Propagation delays, we give  $a = 1111$ ,  $b = 1111$  as well as  $c_{in} = 1$  which is usually 0 for normal adder applications. From this we get output  $s = 11111$ . Here, we see the delays of all sum and final carry unit:


tpd_s0	= 4.499356e-11	targ= 5.049994e-09	trig= 5.005000e-09
tpd_s1	= 4.884426e-10	targ= 5.493443e-09	trig= 5.005000e-09
tpd_s2	= 8.601897e-10	targ= 5.865190e-09	trig= 5.005000e-09
tpd_s3	= 8.515328e-10	targ= 5.856533e-09	trig= 5.005000e-09
tpd_carry	= 7.508256e-10	targ= 5.755826e-09	trig= 5.005000e-09

Fig. 8:  $t_{pd}$  for all  $S_i$  and  $C_{out}$

From this we get  $t_{pd_{min}} = 44.9ps$  and  $t_{pd_{max}} = 0.86ns$
 
### B. D-Flipflop

For D-flipflop (+ve edged), we get the following simulation:



(a) Simulation for min  $t_{pcq}$

(b) Simulation for max  $t_{pcq}$

Fig. 9: Ngspice Simulation for D-FlipFlop

As we can see,  $Q$  is updated to  $D$  at +ve edge only. Hence its working properly.

## IV. SETUP TIME, HOLD TIME AND PROPAGATION DELAY FROM CLK TO Q IN FLIPFLOP

We have used TSPC topology for our D-FlipFlop. Since there is no use of  $\overline{clk}$ , we have zero hold time ( $t_{hold} = 0$ ).

For setup time, we did trial and error and found it to be  $t_{setup} = 0.11ns$ . Any input given less than  $t_{setup}$  before next +ve edge, either input is not registered or output is being corrupted.

For propagation delay from  $clk$  to  $Q$  ( $t_{pcq}$ ), we can see the minimum and maximum  $t_{pcq}$  in Fig. 9. The values are as follows:

tpcq_r	= 1.603094e-10	targ= 5.175309e-09	trig= 5.015000e-09
tpcq_f	= 1.133761e-10	targ= 1.512838e-08	trig= 1.501500e-08
tpcq	= 1.36843e-10		

(a)  $t_{pcq_{min}}$

tpcq_r	= 2.335070e-10	targ= 5.248507e-09	trig= 5.015000e-09
tpcq_f	= 1.819591e-10	targ= 1.519696e-08	trig= 1.501500e-08
tpcq	= 2.07733e-10		

(b)  $t_{pcq_{max}}$

Fig. 10:  $t_{pcq}$  for D-Flipflop

We get  $t_{pcq_{min}} = 0.136ns$  and  $t_{pcq_{max}} = 0.207ns$ .

## V. STICK DIAGRAMS FOR ALL UNIQUE GATES AND FLIPFLOPS

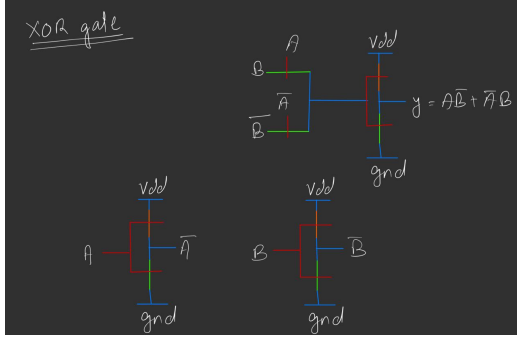


Fig. 11: Stick Diagram for XOR and Inverter

 


Fig. 12: Stick Diagram for AND

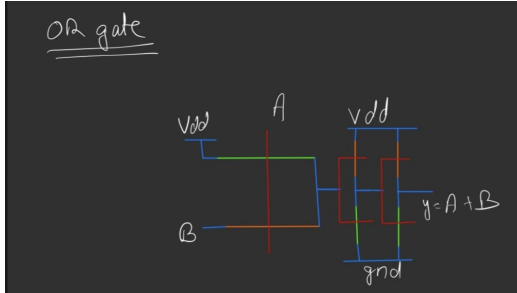


Fig. 13: Stick Diagram for OR

 


Fig. 14: Stick Diagram for D-FlipFlop

## VI. POST LAYOUT SIMULATIONS

### A. D-FlipFlop


 


Fig. 15: Magic Layout for D-FlipFlop

 Here we make the circuit given in Fig. 6 in MAGIC Layout and perform post-Layout simulations.



(a) Simulation for min  $t_{pcq}$

(b) Simulation for max  $t_{pcq}$

Fig. 16: Post-Layout Simulations for D-FlipFlop

Here we can see that we get similar output as pre-layout simulations. However, we have slightly different  $t_{pcq}$ .

tpcq_r	= 1.690262e-10	targ= 5.184026e-09	trig= 5.015000e-09
tpcq_f	= 1.188576e-10	targ= 1.513386e-08	trig= 1.501500e-08
tpcq	= 1.43942e-10		

(a)  $t_{pcq_{min}}$  for Post-Layout

tpcq_r	= 3.889382e-10	targ= 5.403938e-09	trig= 5.015000e-09
tpcq_f	= 1.873369e-10	targ= 1.520234e-08	trig= 1.501500e-08
tpcq	= 2.88138e-10		

(b)  $t_{pcq_{max}}$  for Post-Layout

Fig. 17:  $t_{pcq}$  for D-Flipflop

	Pre-Layout	Post-Layout
$t_{pcq_{min}}$	0.136ns	0.144ns
$t_{pcq_{max}}$	0.207ns	0.288ns

TABLE I: Comparison between pre and post layout simulations

## B. CLA-Adder

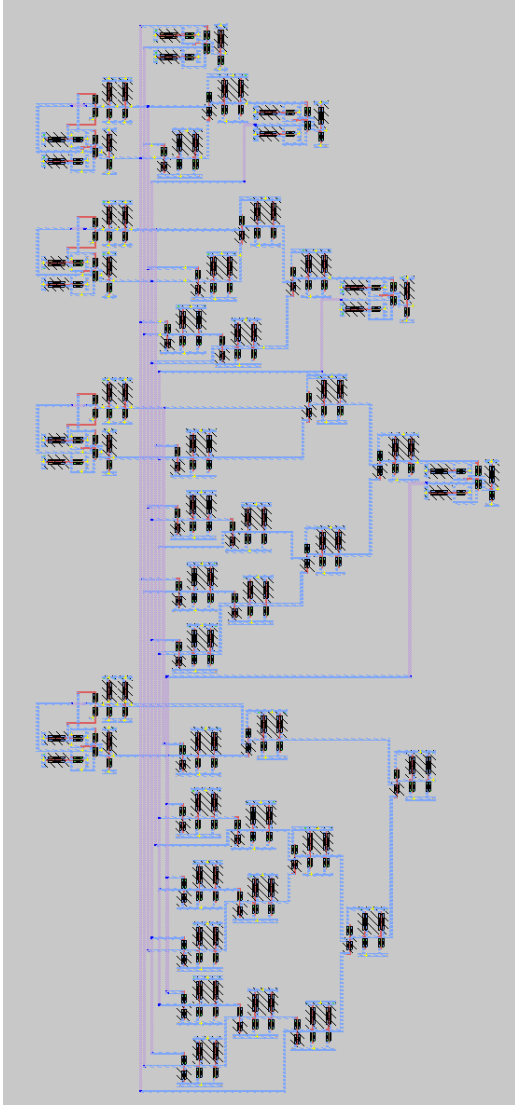


Fig. 18: Magic Layout for CLA-Adder

Here we make the circuit given in Fig. 2 in MAGIC Layout and perform post-Layout simulations. We again perform simulation with input  $a = 1001$  and  $b = 1101$  at  $t=5ns$  and get the following result:

 


Fig. 19: Final output for post-layout

As we can see, with some delay, we get the final output  $s = 10110$  which is same as pre-layout simulations. By giving  $a$  and  $b$  as 1111 as well as  $c_{in} = 1$  for  $s = 1111$ , we get

tpd_s0	= 7.954170e-11	targ= 5.084542e-09	trig= 5.005000e-09
tpd_s1	= 5.824552e-10	targ= 5.587455e-09	trig= 5.005000e-09
tpd_s2	= 6.905608e-10	targ= 5.695561e-09	trig= 5.005000e-09
tpd_s3	= 6.639990e-10	targ= 5.668999e-09	trig= 5.005000e-09
tpd_carry	= 5.585690e-10	targ= 5.563569e-09	trig= 5.005000e-09

Fig. 20: Post-layout delays for all  $s_i$ 's and final carry


Now comparing delays with pre-layout simulations, we get:

	Pre-Layout	Post-Layout
$t_{pd_{min}}$	44.9ps	79.54ps
$t_{pd_{max}}$	0.86ns	0.690ns

TABLE II: Comparison between pre and post layout simulations
 
## VII. SIMULATIONS OF FINAL CIRCUIT IN NGSPICE

We combine the CLA-Adder with D-FlipFlops to give input at positive edge and get output as second positive edge. We give the previous inputs  $a = 1101$  and  $b = 1001$  at first positive edge as shown:



(a)  $a = 1101$

(b)  $b = 1001$

Fig. 21: Inputs for our final adder

We get the following output:

 


Fig. 22: Final output at second +ve edge

As we can see, we get final output as 10110 at the second +ve edge of the clock. This means that our final circuit is working perfectly fine.

Our worst case delay as seen in pre-layout simulations is  $t_{pd_{max}} = 0.86ns$  and for maximum clock frequency at which the circuit works perfectly fine is 833.33MHz or minimum time period of 1.2ns. We can verify this with our theoretical calculations that is

$$t_{clk_{min}} = t_{setup} + t_{pd_{max}} + t_{pcq_{max}}$$

$$t_{clk_{min}} = 0.11ns + 0.86ns + 0.207ns = 1.177ns$$

Now  $t=1.2ns$  is very close to  $1.177ns$ . Hence at  $f_{max} = 833.33MHz$ , our circuit works perfectly. We can see this in simulations as well.

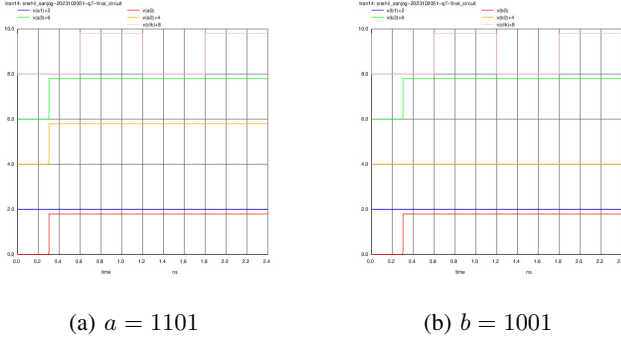


Fig. 23: Inputs for our final adder at maximum clock frequency

 


Fig. 24: Final output at second +ve edge for maximum clock frequency

With less than  $0.2ns$  as  $t_{pcq}$ , we can see the correct output at second +ve edge.

### VIII. FLOOR PLAN AND MAGIC LAYOUT FOR FINAL CIRCUIT

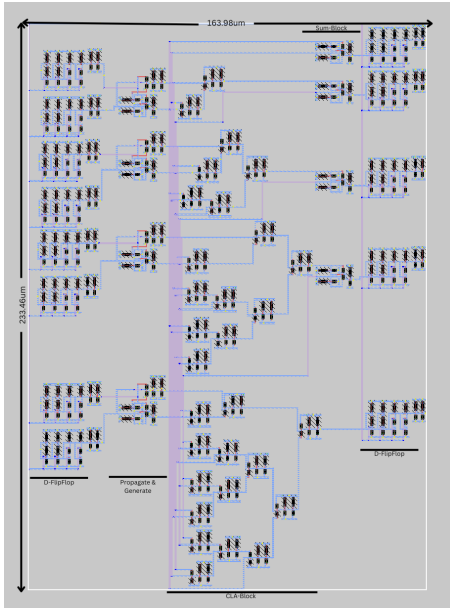


Fig. 25: Complete Floor Plan for Final Circuit

This is the complete floor plan of final circuit with Horizontal Pitch  $163.98\mu m$ , Vertical Pitch  $233.46\mu m$  and total area  $38232.77\mu m^2$ .

### IX. POST LAYOUT SIMULATIONS OF FINAL CIRCUIT

We again give  $a = 1001$  and  $b = 1101$  as input at first +ve edge.

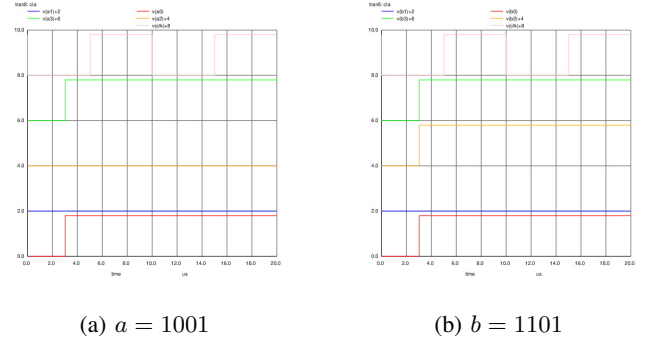


Fig. 26: Inputs for our final circuit

We get the output as follows:

 


Fig. 27: Final output at second +ve edge

As we can see, we get output at second +ve edge as  $s=10110$ . So it matches with its pre-layout simulation. Now for maximum clock frequency, we need to find minimum clock time period. We have  $t_{pd_{max}} = 0.690ns$  for CLA-Adder,  $t_{pcq_{max}} = 0.288ns$  and  $t_{setup} = 0.11ns$

$$t_{clk_{min}} = 0.11 + 0.690ns + 0.288ns = 1.088ns$$

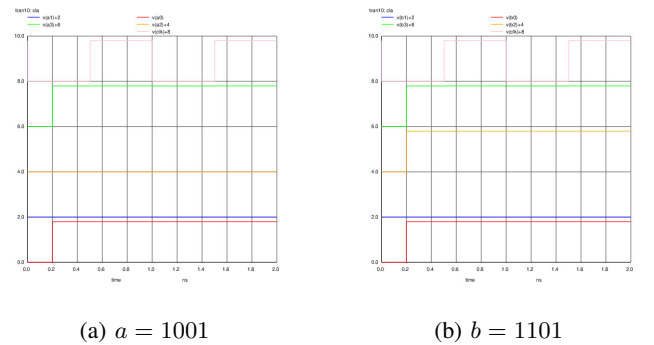


Fig. 28: Inputs for our final circuit at maximum clock frequency

We get the output as follows:



 


Fig. 29: Final output at maximum clock frequency

We get proper output at  $t_{clk} = 1ns$  which is nearly as same as our theoretical minimum value. So,  $f_{max} = 1000MHz$  is the maximum clock frequency.

	Pre-Layout	Post-Layout
$t_{pd_{max}}$	0.86ns	0.690ns
$t_{clk_{min}}$	1.2ns	1ns
$f_{clk_{max}}$	833.33MHz	1000MHz

TABLE III: Comparison between pre and post layout simulations

## X. VERILOG SIMULATIONS AND WAVEFORMS

Now, we create the final CLA Circuit in verilog. We give two inputs,  $a = 1001$ ,  $b = 1101$  and  $a = 1010$ ,  $b = 01101$ . We get the following output:

```
[Running] tb.v
VCD info: dumpfile tb.vcd opened for output.
a=1001 b=1101    cout=x s=xxxx
a=1010 b=0101    cout=1 s=0110
a=0000 b=0000    cout=0 s=1111
a=0000 b=0000    cout=0 s=0000
tb.v:27: $finish called at 43 (1s)
[Done] exit with code=0 in 0.038 seconds
```

Fig. 30: Verilog Output for the above inputs

As we can see, when we give the input, we get the output in the next cycle. We get  $sum=10110$  and  $sum=01111$  after the next input has been given, that is, in the next +ve edge of the clock. In GTKWave, we get the following waveforms:

 


Fig. 31: GTK waveforms for the given inputs

## XI. FPGA AND HARDWARE SIMULATIONS

Now, we give inputs in FPGA board and get the output as shown:

 


Fig. 32: Output on FPGA Board

For a complete video, here is the link:

<https://drive.google.com/file/d/1b7-uLKQ62djXwmcyypvaVRPbVqIZsADK0/view?usp=drivesdk>

We then give the input  $a=1001$  and  $b=1101$  and finally get the output  $S = 10110$  in the oscilloscope:

 


Fig. 33: Output in Oscilloscope

## Individual Oscilloscope Readings:

 


Fig. 34:  $C_{out}$

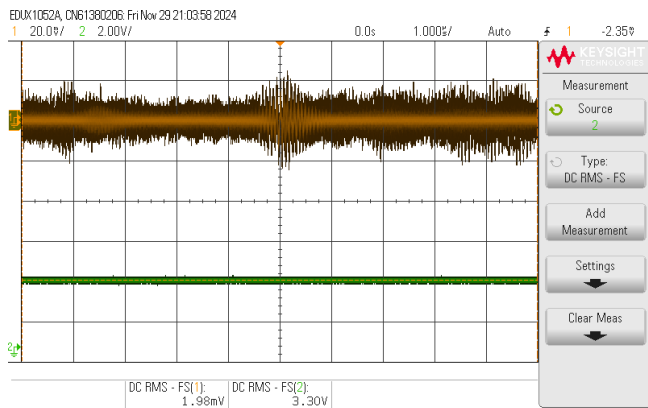


Fig. 35:  $s_3$  and  $s_2$

 


Fig. 36:  $s_1$  and  $s_0$

As we can see, we are getting 3.3V for HIGH (bit 1) and some noise (in mV) for LOW (bit 0). Here we also are getting the sum as 10110.

## XII. CONCLUSION

So, like this, we are able to design a CLA Adder which takes input at one +ve edge and gives output at next +ve edge clock. This makes sure that the CLA adder has enough time to calculate the sum bits.

## REFERENCES

- [1] CMOS VLSI Design (fourth edition) by Weste and Harris.
- [2] Digital Logic and Computer Design by Morris Mano.
- [3] Verilog HDL - Samir Palnitkar
- [4] Internet - Google